

RAJIV GANDHI UNIVERSITY OF KNOWLEDGE TECHNOLOGIES

Department of
Electronics & Communication Engineering



ANALOG ELECTRONIC CIRCUITS LAB

INDEX

- 1. LIST OF EXPERIMENTS.**
- 2. LIST OF EQUIPMENTS.**
- 3. LAB MANUAL.**
- 4. PROCEDURE**
- 5. LAB STAFF.**

I. LIST OF EXPERIMENTS:--

1. D.C. characterization and finding ac model parameters of a BJT.
2. D.C. characterization and finding ac model parameters of a MOSFET.
3. Design of feedback amplifiers with BJT.
4. Design of amplifiers with MOSFET.
5. Design and characterization of simple current mirror circuits using BJT and MOSFET.
6. Design and characterization of cascode current mirror circuits using BJT and MOSFET.
7. Design of Common collector amplifier
8. Design of differential amplifier using BJT with resistive load.
9. Design of differential amplifier using MOSFET with active load.

II.LIST OF EQUIPMENT:-

| SLNO | NAME | RANGE | QUANTITY | DATE OF ARRIVAL |
|------|--------------------|----------------------|----------|-----------------|
| 1 | Digital CRO | | 26 | 01/07/11 |
| 2 | RPS | | 24 | 29/06/11 |
| 3 | Function Generator | 3MHz-With Modulation | 26 | 22/06/11 |
| 4 | Multimeter | MASTECH | 34 | 28/07/11 |
| 5 | Bread board | ----- | 31 | 28/07/11 |
| 6 | CRO demonstrator | 20 MHz-Dual channel | 1 | 22/06/11 |
| 7 | Tables | | 12 | 04/08/11 |
| 8 | Faculty chair | | 1 | 12/09/11 |
| 9 | Student stools | | 25 | 12/09/11 |

Procedure Followed in Lab:

Arrangement in the lab:

Equipment is arranged on the table in such a way that two batches of students can use a single table. Students are divided into batches of three. So on each table 6 students would be working. (Separate equipment for separate batches)

What is expected from the student?

Dress code has to be strictly followed in the lab. The lab is totally of 3 hrs duration during which the student is expected to finish the experiment. Each and every student should submit their report of the previous experiment. Every student has to have an idea over the experiment that is to be done in that session. With that he/she has to prepare a list of the equipment necessary which is to be submitted to the particular lab assistant.

Role of the Lab assistant:

Lab assistant would take attendance right at the beginning of the session. He/she has to check if everyone has submitted their report. Later after the students submit their list of equipment he/she should acknowledge the list provided by the students and provide them with the Equipment. While students do the experiment if they have any problem or doubt, Lab assistants would clarify it. Lab assistants would help them during the entire session in doing the experiment.

III. LAB MANUAL

Experiment no:1

DC CHARACTERIZATION AND FINDING AC MODEL PARAMETERS OF A BJT

AIM: a) To obtain common emitter characteristics of npn transistor
b) To find ac model parameters of BJT

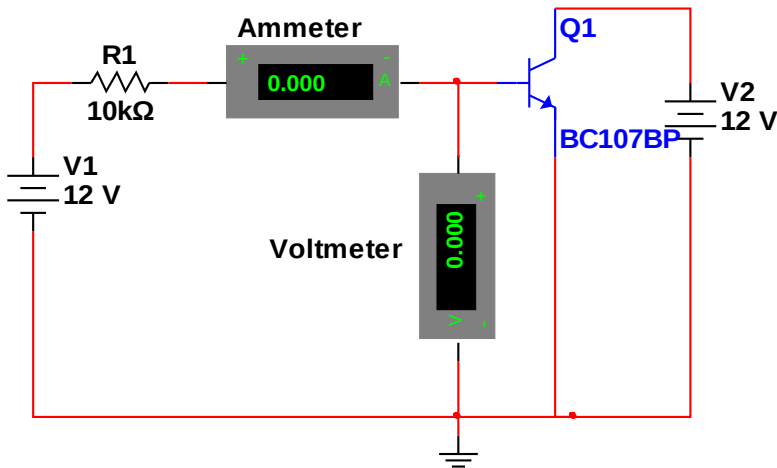


Figure 1.1

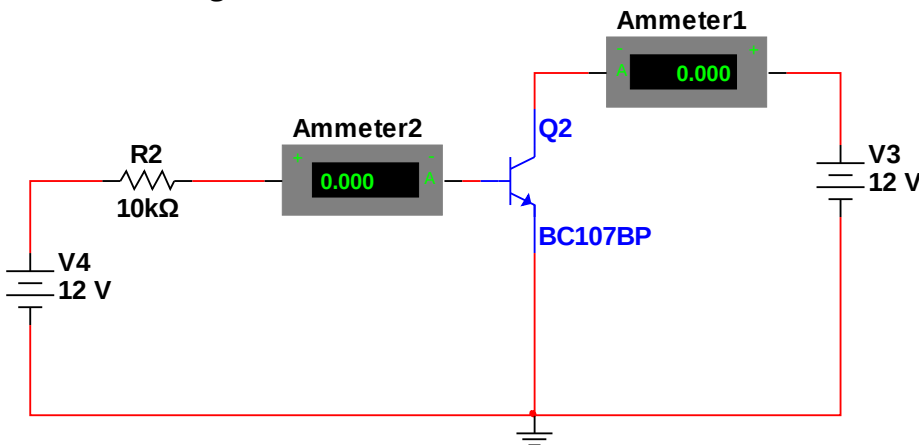


Figure 1.2

Theory:

Transistor is an active three terminal device. The three terminals are collector, base and emitter. We can connect these three terminals in three different configurations. When emitter is common to both input and output ports, this type of configuration is known as common emitter. Input is applied to base and output is taken from collector side.

Input characteristics are obtained by keeping V_{CE} constant and varying V_{BE} and measuring I_B value. Input characteristics are drawn by keeping V_{CE} constant where for a small change in V_{BE} I_B changes to sudden increment that voltage known as cut-in voltage.

Output characteristics will be obtained by keeping I_B constant and plot V_{CE} Vs I_C after certain V_{CE} , I_C will increase very slowly and saturates

Procedure:-

- a) connect the circuit as per the diagram .
- b) By keeping $V_{CE}=0$ vary the V_{BE} voltage and observe the corresponding I_B Values.
- c) Tabulate measured values.
- d) Repeat the above steps for different values of V_{CE}
- e) Plot the graph between V_{BE} and I_B

For output Characteristics:

- a) connect the circuit as per the diagram .
- b) By keeping I_B vary the V_{CE} voltage and observe the corresponding I_C Values.
- c) Tabulate measured values.
- d) Repeat the above steps for different values of V_{CE}
- e) Plot the graph between V_{CE} and I_C at a constant value of I_B .


Result:

Experiment no:2

DESIGN OF COMMON EMITTER AMPLIFIER

Aim:-

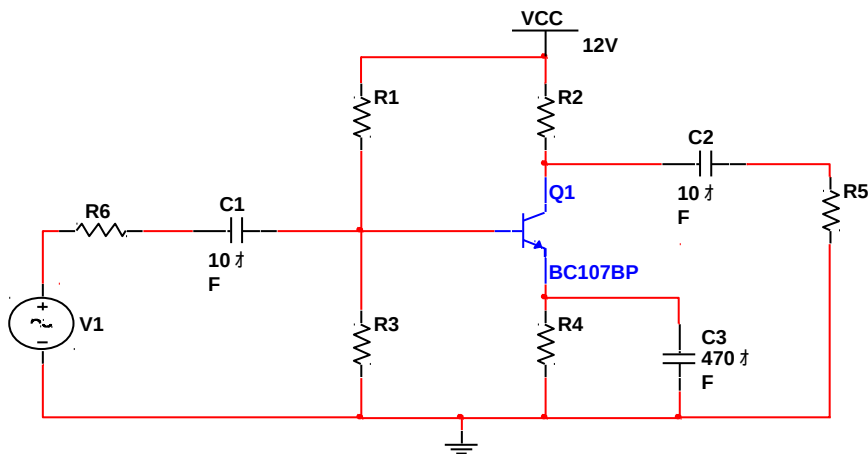To design CE amplifier to find the frequency response of CE amplifier.



Theory:-

It has moderately low input resistance
its output resistance is moderately large
its current gain is high
it has very high voltage gain in the order of 1500 or so.
It produces very high power gain in the order of 10,000
it produces phase reversal of input signal.

Designing procedure:-

Let $V_{CC}=12\text{V}$

$$V_{CE} \leq V_{CC}/2$$

$$V_E \leq V_{CC}/10$$

Let $I_E=2\text{mA}$

$$R_E = V_E / I_E$$

$$R_C = (V_{CC} - V_{CE} - V_E) / I_C$$

$$V_B = V_{BE} + V_E$$

PROCEDURE:-

- 1) Take the components according to the theoretical design values.
- 2) connect the circuit as per the ckt diagram.
- 3) Apply DC input to circuit and measure the DC conditions and note down the values.
- 4) Apply AC signal using function generator and connect the output across the

collector resistor R_C

- 5) measure the output signal value and calculate the gain.
- 6) Keep the input voltage to any constant value within the range vary the frequency to a certain range.
- 7) Notedown the output values and tabulate them.
- 8) Plot frequency Vs gain.


Result:

Experiment no:3

DESIGN OF COMMON COLLECTOR AMPLIFIER

Aim:-

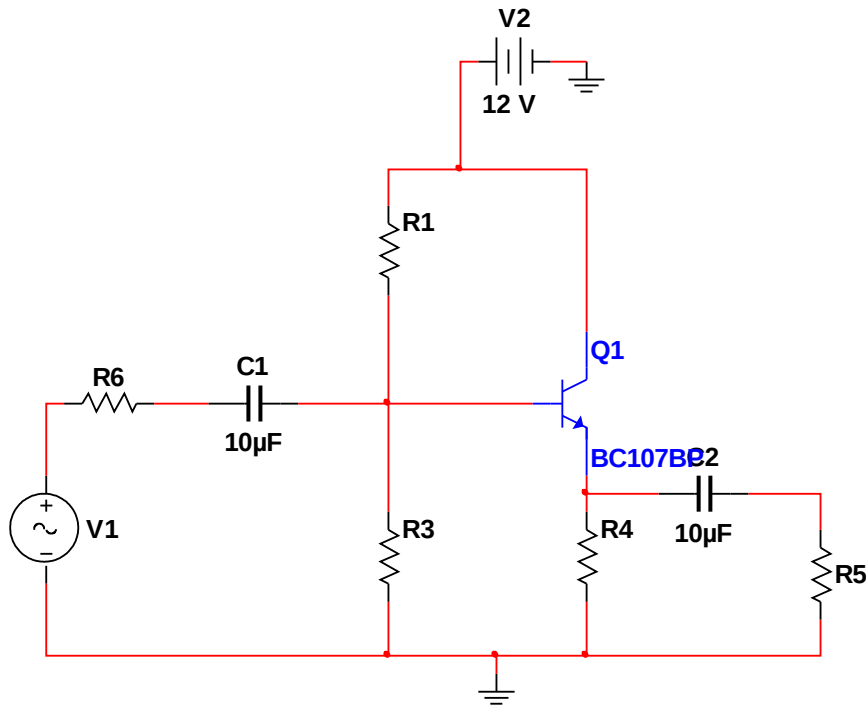To design CC amplifier to find the frequency response.



Theory:-

It has high input resistance.

its output resistance is low.

its current gain is high

it has very high voltage gain less than 1.

It produces very high power gain in the order of 10 to 20 dB

Designing procedure:-

$$V_{CC} = 12V$$

$$\text{Let } (I_C, V_{CE}) = (2\text{mA}, 5V)$$

$$R_E = \frac{V_{CC} - V_{CE}}{I_C}$$

$$\frac{V_{CC} \times R_2}{R_1 + R_2} = V_{Th}$$

$$R_i = R_{Th} \parallel \beta(r_e + R_E)$$

PROCEDURE:-

- 1) Take the components according to the theoretical design values.

- 2) connect the circuit as per the ckt diagram.
- 3) Apply DC input to circuit and measure the DC conditions and notedown the values.
- 4) Apply AC signal using function generator and connect the output across the collector resistor R_C
- 5) Measure the output signal value and calculate the gain.
- 6) Keep the input voltage to any constant value within the range vary the frequency to a certain range.
- 7) Notedown the output values and tabulate them.
- 8) Plot frequency Vs gain.

Result:-

Experiment no:4

DESIGN OF DIFFERENTIAL AMPLIFIER USING BJT WITH RESISTIVE LOAD.

Aim:-

To design differential amplifier using BJT with resistive load and to find out single ended output, differential output, frequency response, and A_d , A_c and CMRR.

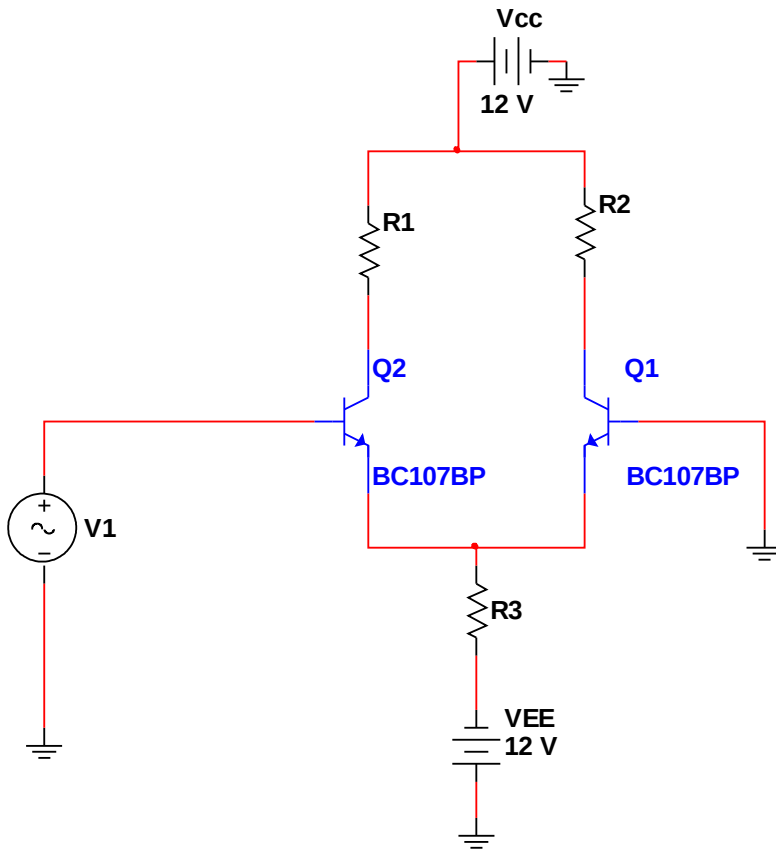


Figure 4.1

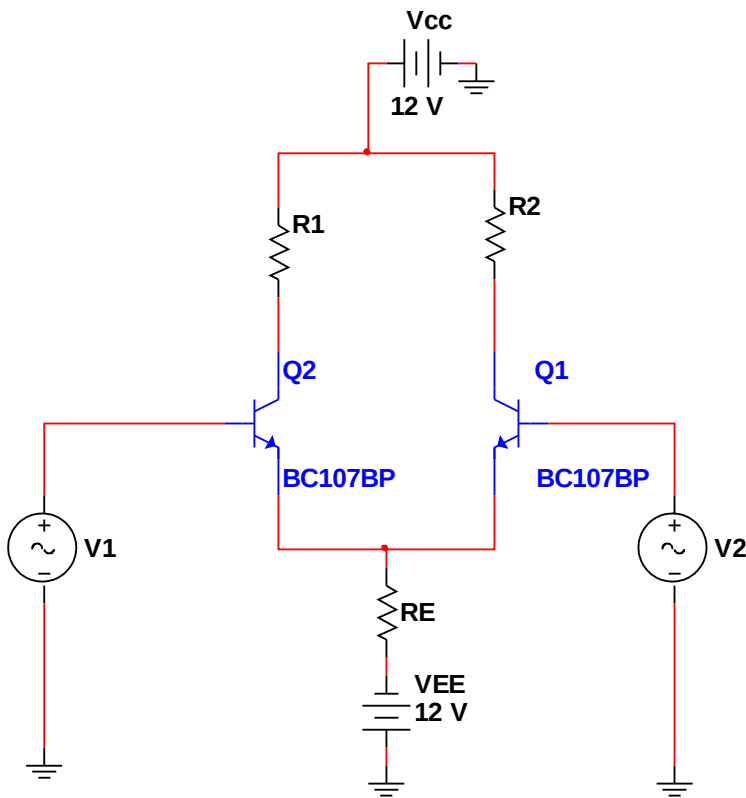


Figure 4.2

Theory:-

The differential amplifier is the basis for the operational amplifier which has very high input resistance and gain.

The usefulness of differential pair stems from two properties: cascades of differential pairs can be directly connected to one another without interstage coupling capacitors.

To increase the range of differential mode input over which the emitter-coupled pair behaves approximately as a linear amplifier, emitter degeneration resistors are frequently included in series with the emitter of transistors.

Designing procedure:-

$$V_{CC} = V_{EE} = 12V$$

$$\text{Let } (V_{CB}, I_C) = (5V, 0.5mA)$$

$$I_O = I_{E1} + I_{E2}$$

$$R_E = \frac{V_{EE} - V_Y}{I_O}$$

$$A_d = \frac{-g_m R_C}{2}$$

$$A_c = \frac{-R_C}{r_e + 2R_E}$$

Procedure:-

- 1) Check the given equipment whether they are working properly or not and connect the circuit as shown in fig.
- 2) Set the DC voltages from DRPS and measure the DC conditions of the circuit.
- 3) Feed the differential signal to circuit from function generator and observe the single ended outputs at two output ports on the CRO.
- 4) Observe the differential output using math function and note down the values.
- 5) Calculate A_d , observe frequency response and measure signal handling capacity.
- 6) Now feed the common mode signal by connection two base terminals to positive terminal of input and observe the same as that of differential input.
- 7) Calculate the common mode rejection ratio.


Result:-

Experiment no:5

DESIGN OF COMMON SOURCE AMPLIFIER

Aim:-

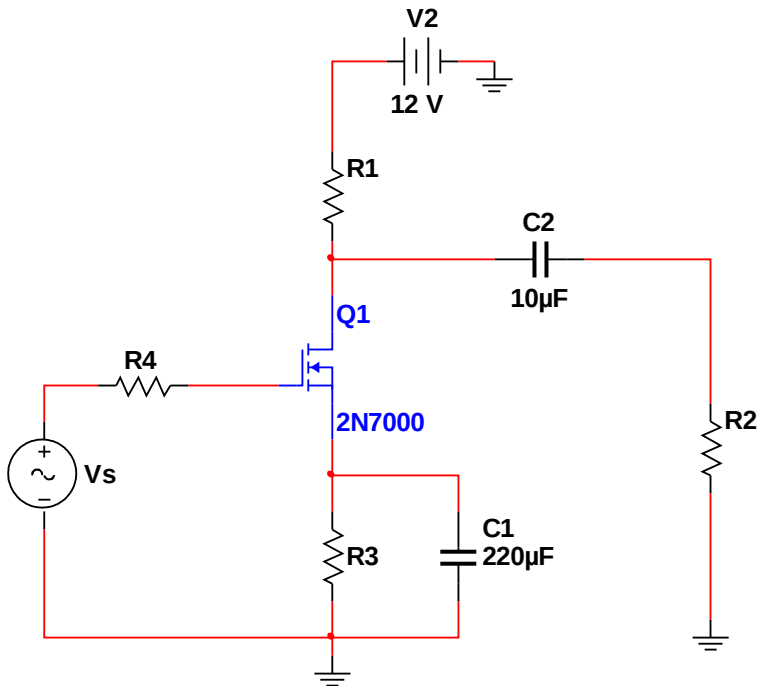To design CS amplifier to find the frequency response.



Designing procedure:-

$$V_{DD} = V_{SS} = 12V$$

$$V_{GS} = \sqrt{\frac{I_{DSQ}}{K}} + V_T$$

$$I_D R_S \gg V_{GS}$$

$$R_D = \frac{V_{DD} - V_{DG}}{I_D}$$

$$R_S = \frac{V_{SS} - V_{GS}}{I_D}$$

PROCEDURE:-

- 1) Take the components according to the theoretical design values.
- 2) Connect the circuit as per the ckt diagram.
- 3) Apply DC input to circuit and measure the DC conditions and note down the values.
- 4) Apply AC signal using function generator and connect the output across the collector resistor R_C
- 5) Measure the output signal value and calculate the gain.
- 6) Keep the input voltage to any constant value within the range vary the frequency to a certain range.
- 7) Note down the output values and tabulate them.
- 8) Plot frequency Vs gain.


Result:-

Experiment no:6

DESIGN OF DIFFERENTIAL AMPLIFIER USING BJT WITH ACTIVE LOAD.

Aim:-

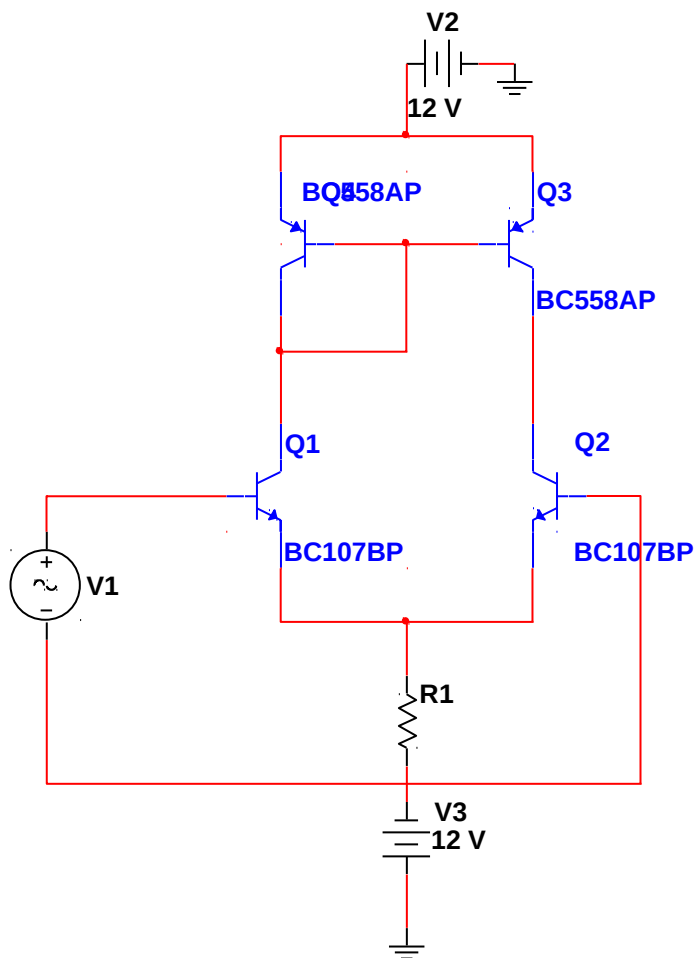To design differential amplifier using BJT with active load and to find out single ended output, differential output, frequency response, and A_d , A_c and CMRR.



Theory:-

In the active load we use two npn transistors which identical and 2 pnp identical transistors. In differential amplifier R_c is replaced by current mirror circuit which is acting as load. The current mirror circuit itself it contains active elements that's why we call it as active load. By using this active load we can get more differential mode gain and CMRR can be improved.

Designing procedure:-

$$V_{CC} = V_{EE} = 12V$$

$$I_{E1} = I_{E2} = 1mA$$

$$I_O = I_{E1} + I_{E2}$$

$$R_E = \frac{V_{EE} - V_{BE}}{I_O}$$

PROCEDURE:-

- 1) Connect the circuit as per the ckt diagram.
- 2) Apply DC input to circuit and measure the DC conditions and notedown the values.
- 3) Apply AC signal using function generator and connect the output across the collector resistor RC.
 - 4) measure the output signal value and calculate the gain.
- 5) Keep the input voltage to any constant value within the range vary the frequency to a certain range.
 - 6) Notedown the output values and tabulate them.
- 7) Plot frequency Vs gain.


Result:-

Experiment no:7

DESIGN OF FEEDBACK AMPLIFIER USING BJT.

Aim:-

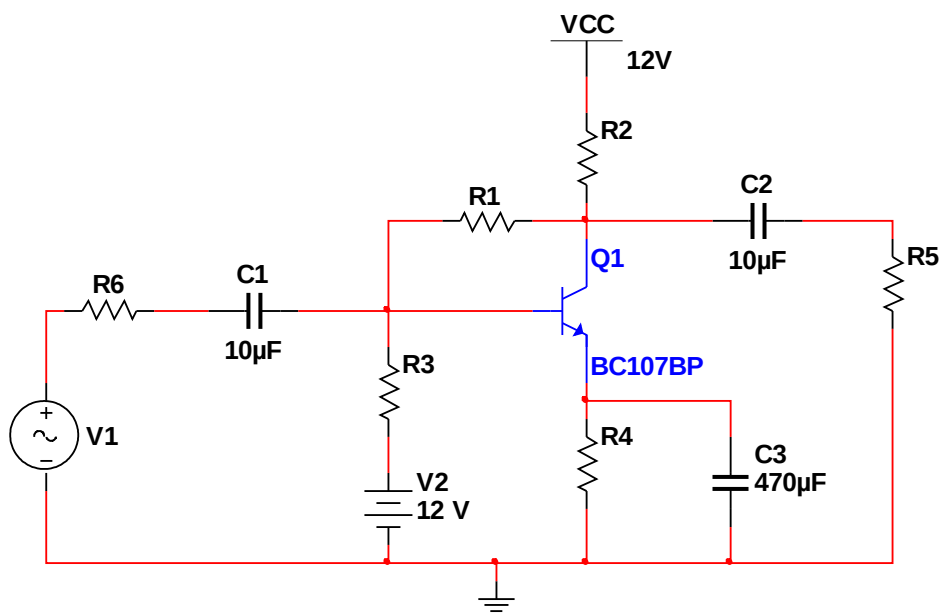To design feedback amplifier with BJT and to find out the gain and frequency response with and without feedback network.



Theory:-

In a feedback amplifier a portion of the amplifier output V_o is connected to the feedback network which provides a reduced portion of the output as a feedback signal to the input mixer network. Depending on the relative polarity of the signal being feedback into a circuit. One may have negative or positive feedback results in decreased voltage gain.

PROCEDURE:-

- 1) Take the components according to the theoretical design values.
- 2) Connect the circuit as per the ckt diagram.
- 3) Apply DC input to circuit and measure the DC conditions and note down the values.
- 4) Apply AC signal using function generator and connect the output across the collector resistor R_C .
- 5) Measure the output signal value and calculate the gain.
- 6) Keep the input voltage to any constant value within the range, vary the frequency to a certain range.
- 7) Note down the output values and tabulate them.

- 8) Plot frequency Vs gain.
- 9) Repeat the steps from 3 to 6 for the network with feedback.
- 10) Compare the results of amplifier with and without feedback network.


Result:-

Experiment no:8

DESIGN AND CHARACTERIZATION OF SIMPLE CURRENT MIRROR CIRCUIT USING BJT.

Aim:-

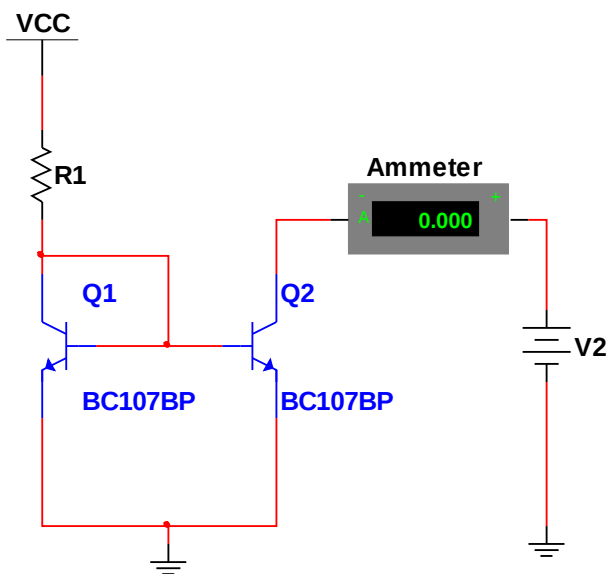- 1) To design simple current mirror circuit using BJT.
- 2) To plot characteristics of simple current mirror circuit and to find the output resistance.



Theory:-

Circuit consisting of two matching transistors with the collector of one connected to the bases of both, thus providing the same collector current in each transistor. Under ideal conditions, the current mirror gain is independent of input frequency and the voltage between the output and common terminals.

Designing procedure:-

$$\text{Let } I = 1\text{mA}, V_{CC} = 6\text{V}$$

$$\frac{V_{CC} - V_{BE}}{I} = R$$

PROCEDURE:-

- 1) connect the circuit as per the ckt diagram

- 2) measure the input current and compare it with I_o .
- 3) Now vary the potentiometer value over the available range.. and measure the corresponding I_o and output voltage V_o values.
- 4) Tabulate the values and plot the graph.
- 5) Now find out the output resistance values from the slope of the graph, it is similar to potentiometer value.


Result:-

Experiment no:9

DESIGN AND CHARACTERIZATION OF CASCODE CURRENT MIRROR CIRCUIT USING BJT.

Aim:-

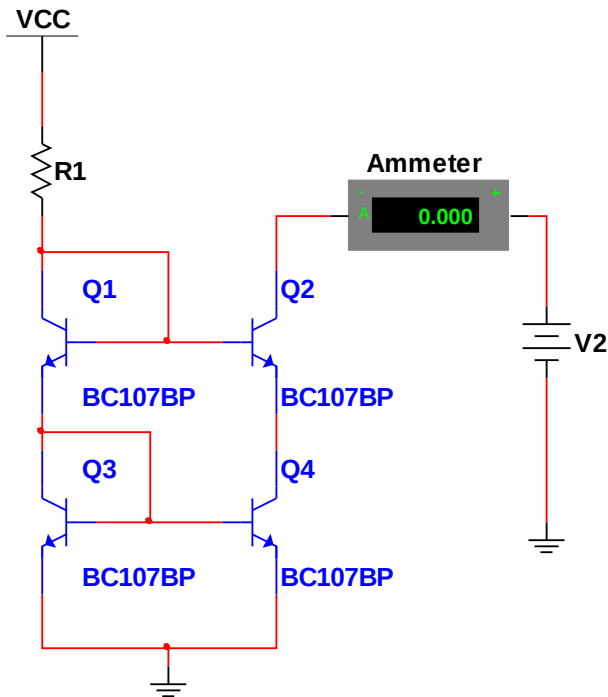To design cascode current mirror circuit using BJT and to plot the characterization of the cascode current mirror.



Theory:-

Cascode is the combination of CE and CB amplifier. Emitter Terminal in the CE Configuration is connected to the emitter of CB.

The Cascode transistor raises the level of output resistance. And the cascoding increases the magnitude of the open circuit voltage. A drawback of the cascode current mirror is that it consumes a relatively large portion of the steadily shrinking supply voltage. The minimum voltage required across the output cascode mirror is 1V, this limits the signal swing at the output of mirror.

Designing procedure:-

Let $I = 1\text{mA}$, $V_{CC} = 6\text{V}$

$$\frac{V_{CC} - 2V_{BE}}{I} = R$$

PROCEDURE:-

- 1) connect the circuit as per the ckt diagram
- 2) measure the input current and compare it with I_o .
- 3) Now vary the potentiometer value over the available range.. and measure the corresponding I_o and output voltage V_o values.
- 4) Tabulate the values and plot the graph.
- 5) Now find out the output resistance values from the slope of the graph, it is similar to potentiometer value.

Result:-

IV.PROCEDURE:-

- a) 70 students are divided into 23 batches with 3 students in each batch.
- b) Labs session are conducted on basis on learning by doing.
- c) every week one experiment is conducted.
- d) students need to submit lab observation while leaving lab in each lab session.
- e) lab reports has to submit every week.

V. STAFF:

LAB INCHARGE:

Lab Assistant: mohd.haneef